



MANIPAL INSTITUTE OF TECHNOLOGY
MANIPAL
(A constituent unit of MAHE, Manipal)

MANIPAL INSTITUTE OF TECHNOLOGY

(A constituent Unit of Manipal Academy of Higher Education)

MANIPAL

Drives, Controls and Modelling Laboratory Manual (MTE 3161)

Fifth Semester B.Tech (Mechatronics Engineering)

NAME: Swaraj Dangare

REG NO: 210929156

ROLL NO: 37

Lab VI:

Date: 26/10/2023

Closed loop Speed Control of DC Motor using buck converter

Aim:



To model armature voltage speed control of DC motor using buck converter.

Problem 1:



A Dc armature controlled motor with the following parameters: $R = 2 \Omega$, $L = 1.1\text{mH}$ and $K_b = 1.26 \text{ V/rad/sec}$, $K_t = 1.26 \text{ N.m/Amp}$, with rotor parameters of $J = 0.05\text{kg-m}^2$, $B = 0 \text{ Nm/rad/sec}$ with no load is directly started from a dc supply voltage of 220V. Plot the motor starting speed response and the time taken to reach 157.07 rad/sec (1500 rpm).

Control the speed of DC motor using armature voltage control through buck converter.



Circuit Description:

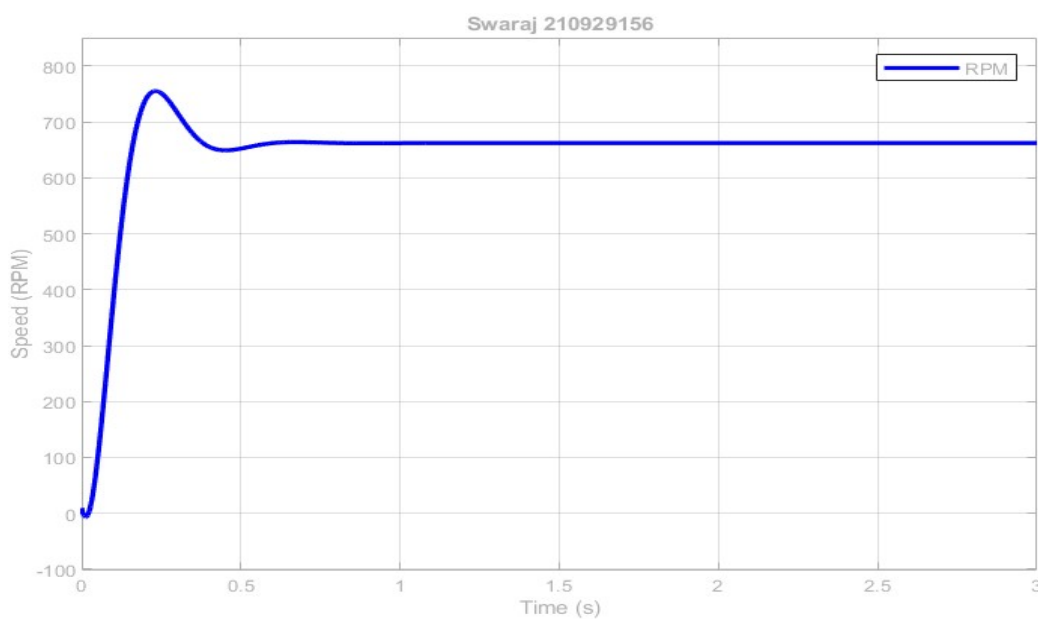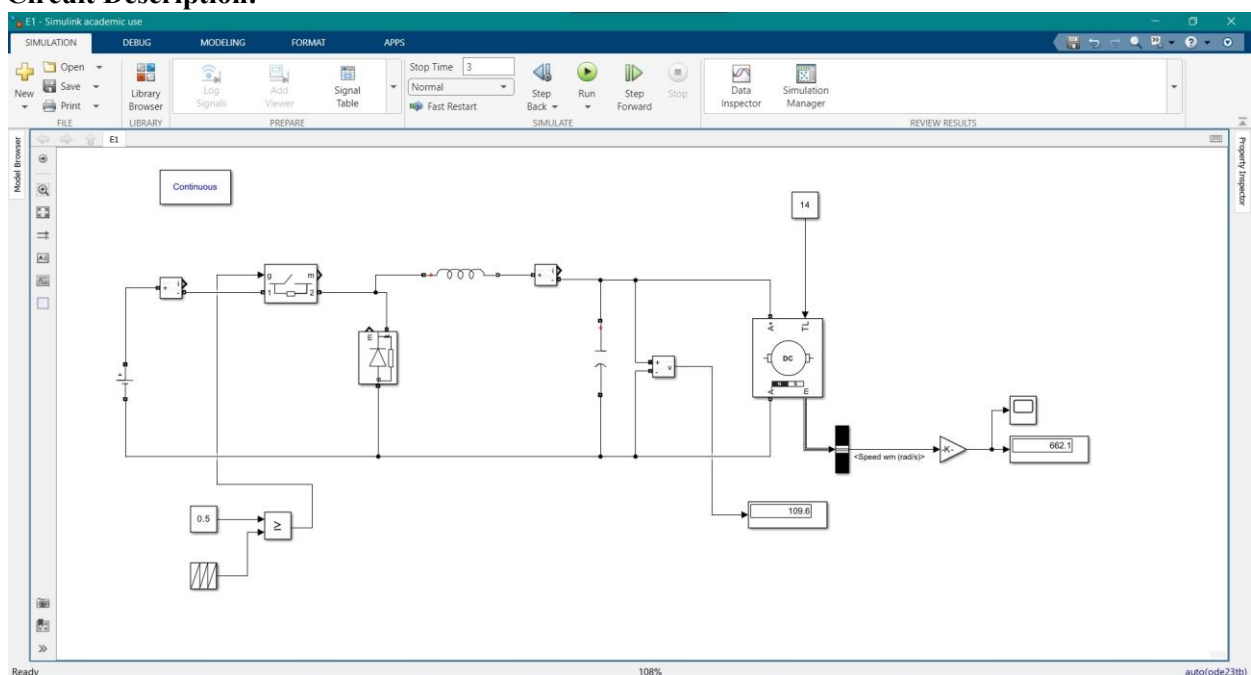

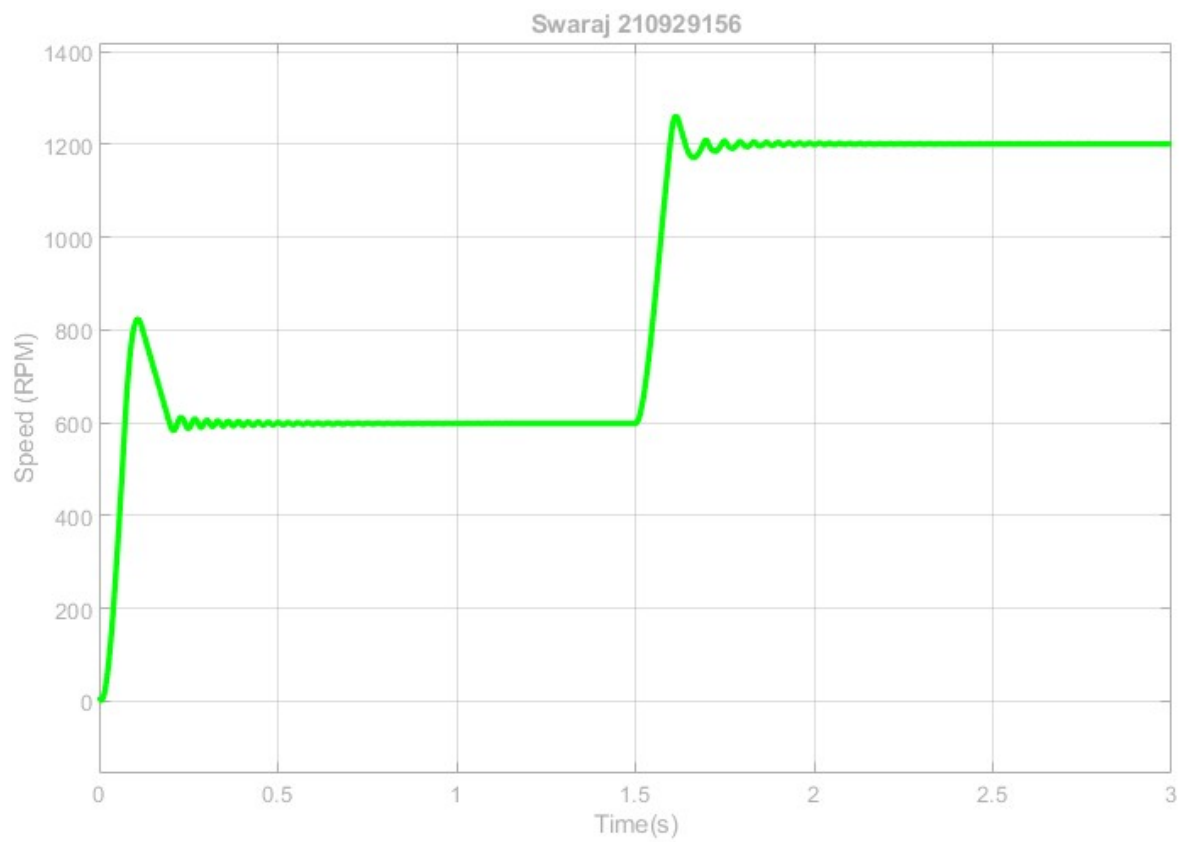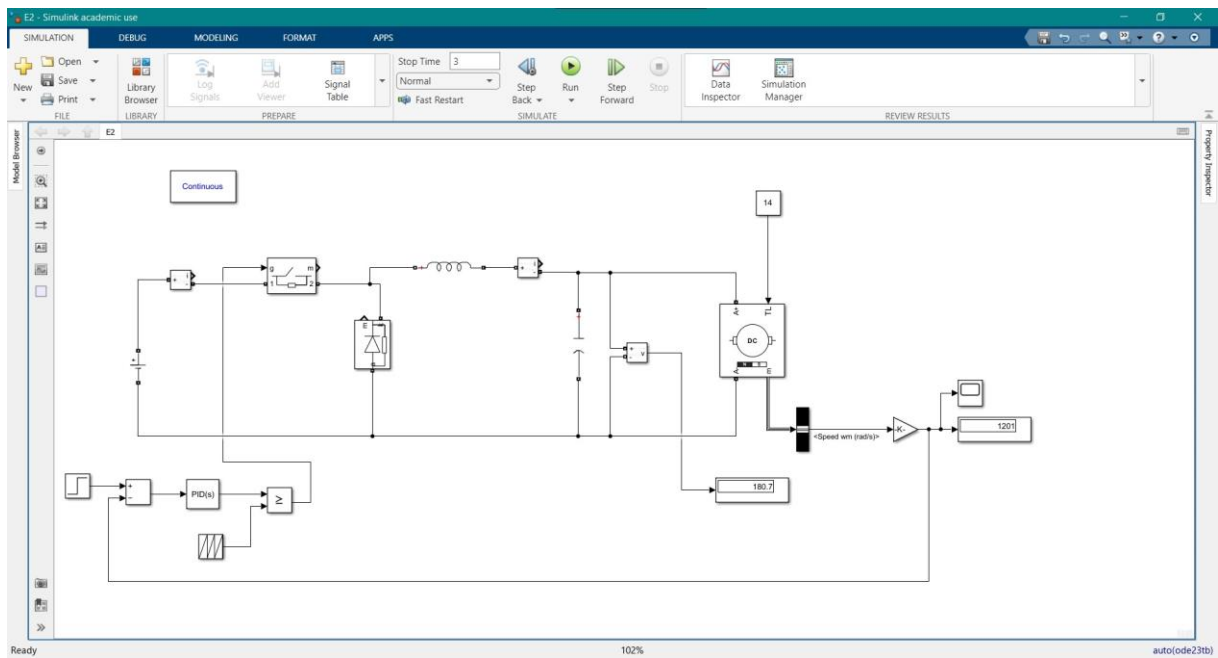Closed loop speed control: $k_p=0.1$ $k_i=0.02$, step change in input reference 600 rpm to 1200 rpm



Closed loop speed control: $k_p=0.1$ $k_i=0.02$, step change in load from 7Nm to 14Nm for constant speed of 1200 rpm.

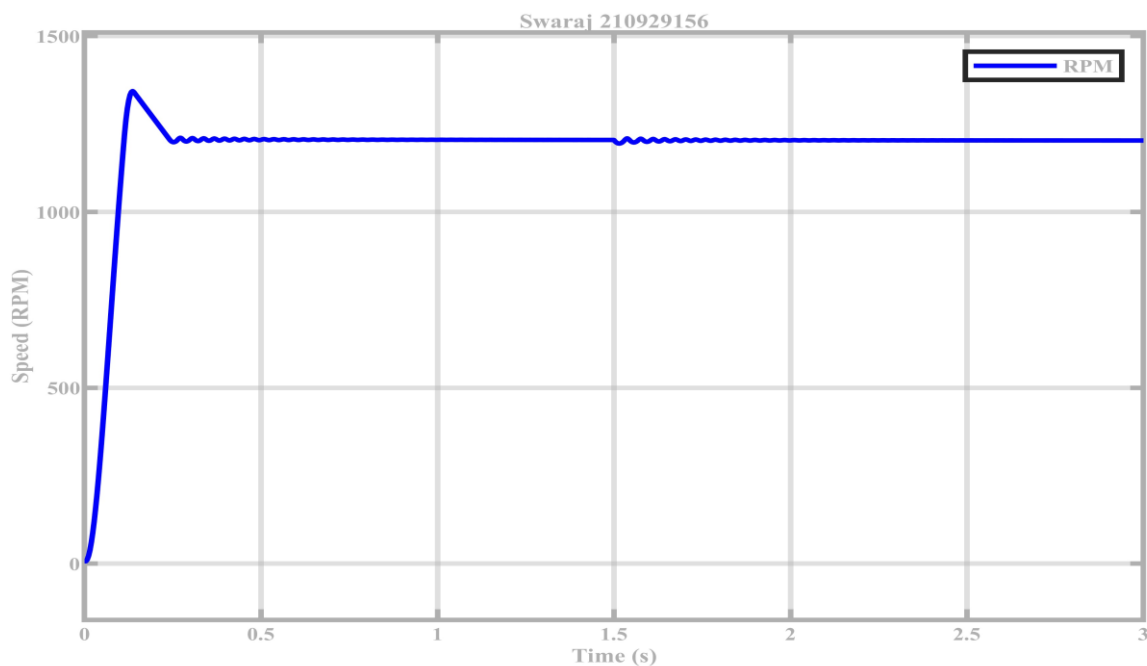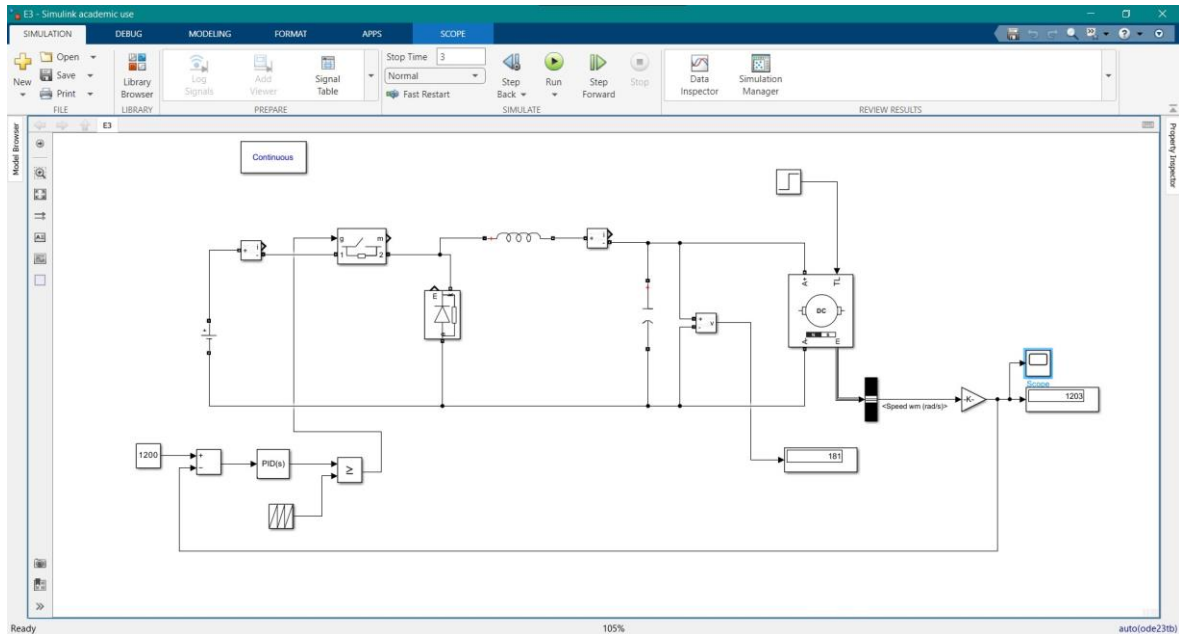




Problem 2:

To model and simulate the DC motor with closed loop speed control with current controller using Simscape. A Dc armature controlled motor with the following parameters: $R = 1.1 \Omega$, $L = 0.003H$ and $K_b = 1.2 V/rad/sec$, $K_t = 1.2 N.m/Amp$, with rotor parameters of $J = 0.05kg-m^2$, $B = 0.001 Nm/rad/sec$. Develop the model and find the speed response with step change in speed and step change in load.

Given:

Speed controller gains: $k_p=0.1$, $k_i=0.1$

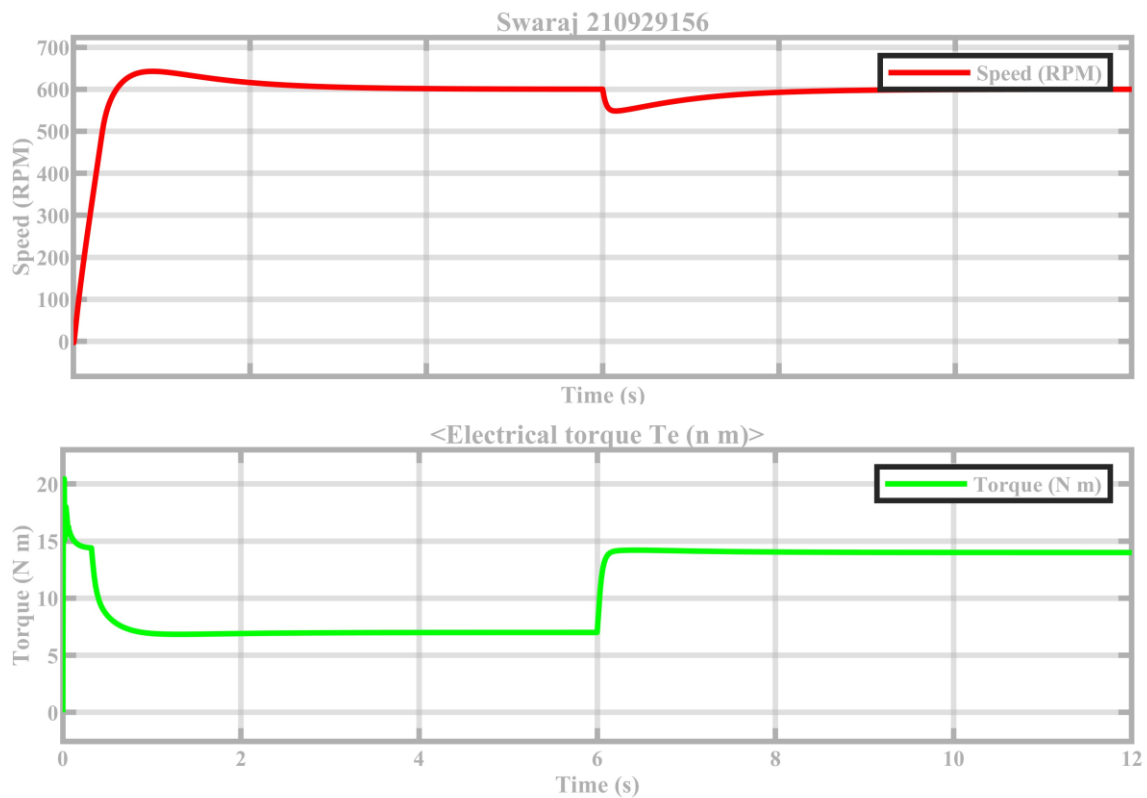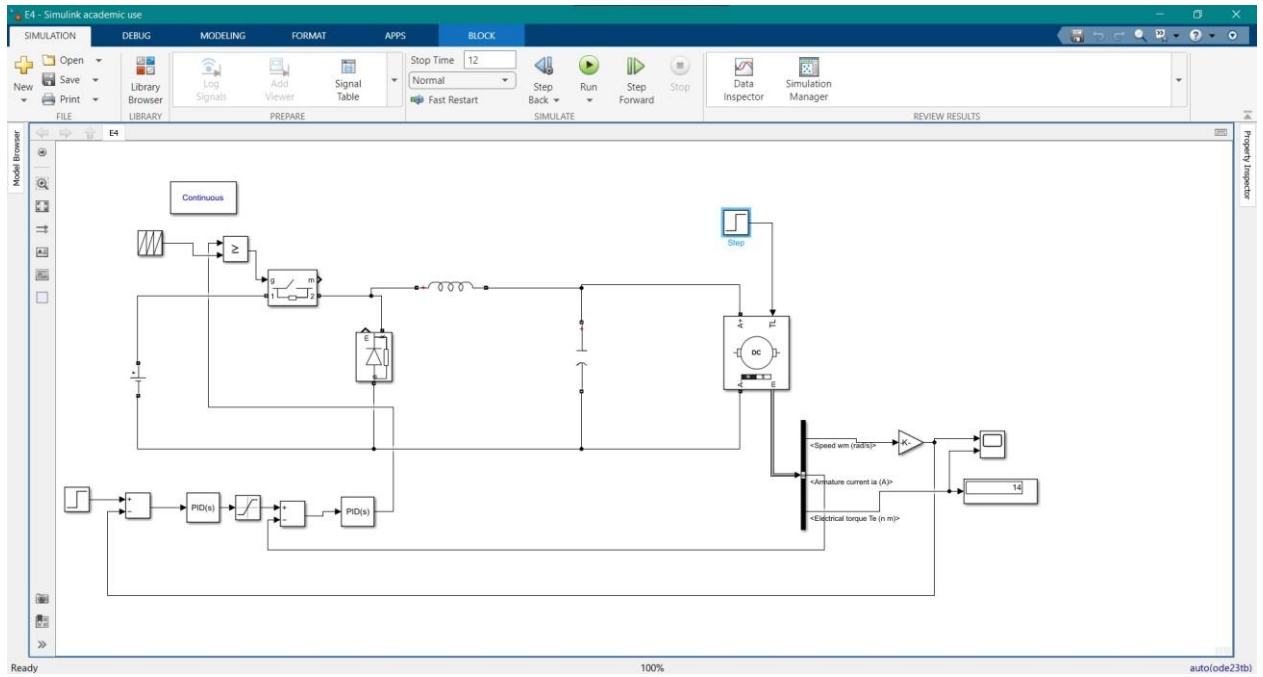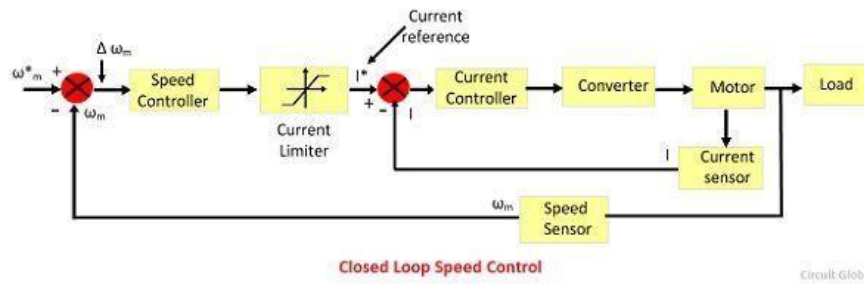Current controller gains: $k_p=0.01$, $k_i=0.08$




Open-Ended Lab Exercises - 5:

1. A DC armature controlled motor with the following parameters: $R = 2\Omega$, $L = 0.011H$ and $K_b = K_t$ 1.26V/rad/sec, with rotor parameters of $J = 0.05 \text{ kg-m}^2$, $B = 0 \text{ Nm/rad/sec}$ with a FAN load with coefficient $5.67e-4$. Calculate the Torque at 750rpm and 1200rpm and simulate the closed loop speed control of Motor with 750rpm for 5 secs and 1200rpm in next 5 secs.

Torque at 750 rpm = 3.5 N.m

Torque at 1200 rpm = 8.97 N.m

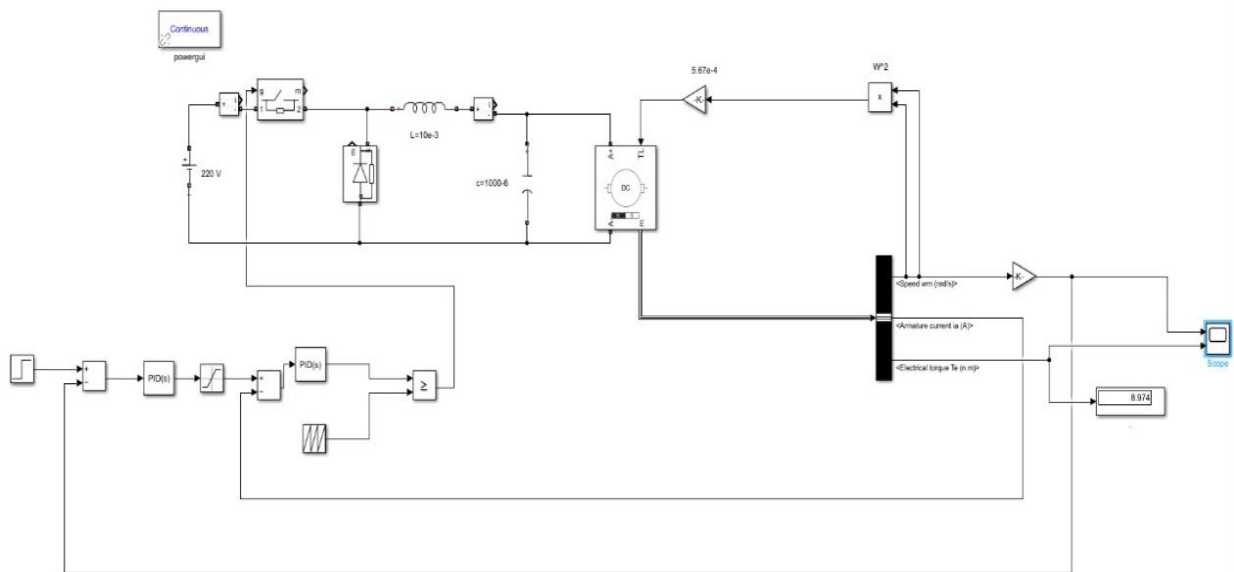

Swaraj 210929156

